

TYPICAL OSCILLATOR CIRCUIT

OSC CELL = oscillator circuit integrated into any IC.

$R_f$  = feedback resistor, sometimes integrated in IC or is required as external resistor

$C_g$  = capacitance of oscillator input

$C_d$  = capacitance of oscillator output

$R_d$  = Phase shift resistor, necessary at lower frequencies to meet oscillation condition that phase shift all the way around the oscillator loop need to add up to 360°.

$Y1$  = Quartz crystal unit

$C1$  and  $C2$  = external load capacitors.

$C_{PCB1}$  and  $C_{PCB2}$  = stray capacitances of PCB traces

The total LOAD CAPACITANCE of the oscillator circuit is the sum of all capacitances, consisting of:

1. The two external capacitors (here called  $C1$  and  $C2$ )
2. The IC input and output capacitances (here called  $C_g$  and  $C_d$ )
3. The stray capacitances of PCB traces (here called  $C_{PCB1}$  and  $C_{PCB2}$ )

Commonly being only the values of the external capacitors known so that a correct calculation of the actual load capacitance is not possible.

In such case we use simplified formula to calculate the load capacitance as:

$$C_{L_{TOTAL}} = \frac{C1 \times C2}{C1 + C2} + C_{STRAY}$$

Here  $C1$  and  $C2$  are the external capacitors in the circuit, values should be known.

$C_{stray}$  is summarized value for IC input and output capacitance and the PCB traces.

$C_{stray}$  in a 3.3VDC circuit is often 3~4pF.

$C_{stray}$  in a 5.0VDC circuit often 5~7pF.


However, we have also seen circuits that had large deviation from these values.

**TOTAL LOAD CAPACITANCE FOR CRYSTAL Y1 IS THE SUM OF:**

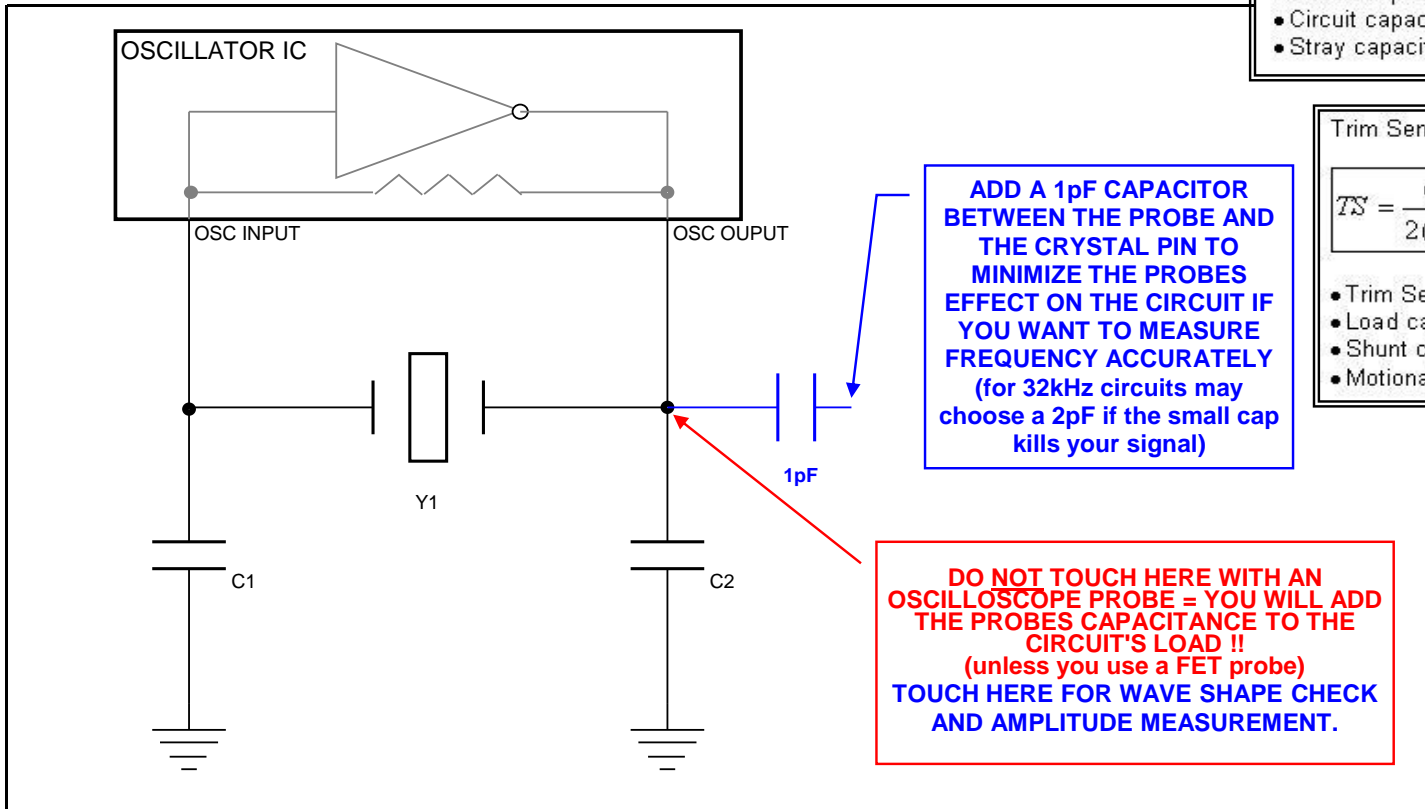- (1) Capacitance of load capacitors C<sub>L1</sub> and C<sub>L2</sub>.
- (2) Capacitance of IC INPUT and OUPUT.
- (3) Stray capacitance of PCB traces.

*Based on the crystals Trim Senisitivity, the frequency will change if total load capacitance changes.*

Typical schematics of a crystal oscillator circuit is shown below.



Total Load Capacitance CL in an oscillator circuit can be calculated as:

$$CL_{TOTAL} = \frac{C1 \times C2}{C1 + C2} + C_{STRAY}$$

- Total load capacitance CL<sub>TOTAL</sub> [pF]
- Circuit capacitor C1 [pF]
- Circuit capacitor C2 [pF]
- Stray capacitance C<sub>STRAY</sub> [pF]

Trim Sensitivity of Quartz Crystal

$$TS = \frac{C_1 \times 1000}{2(C_0 + C_L)^2}$$

- Trim Sensitivity [ppm/pF]
- Load capacitance C<sub>L</sub> [pF]
- Shunt capacitance C<sub>0</sub> [pF]
- Motional capacitance C<sub>1</sub> [fF]