

**Ultra-low Jitter High Frequency
LVDS Clock Oscillators
for Optical DSPs**

Application Guide



LVDS Oscillators

Recommendations for Circuit Configuration, Test Set-Up and Power-Supply Noise Rejection Optimization

Table of Contents

This Application Note is offering recommendations for:

- a) Application circuit configuration and PCB layout recommendations - Page 2
- b) Test set-up: Phase Noise Measurement - Page 6
- c) Test Set-up: Output Signal Integrity - Page 7
- d) Power-supply noise rejection optimization - Page 8


Note:

All circuits and tests described in this Application Note have used Raltron LVDS clock oscillator 2.5 mm x 2.0 mm 2.5 V 20 ppm 156.250 MHz PN [CL2520-156.250-2.5-20-X-T-TR-NS2](#)

This item was used as an example and the same circuits and tests are applicable for the whole family of [Raltron LVDS clock oscillators](#).

Circuit Configuration and PCB Layout Recommendations

Circuit Configuration 0 Complete Circuit

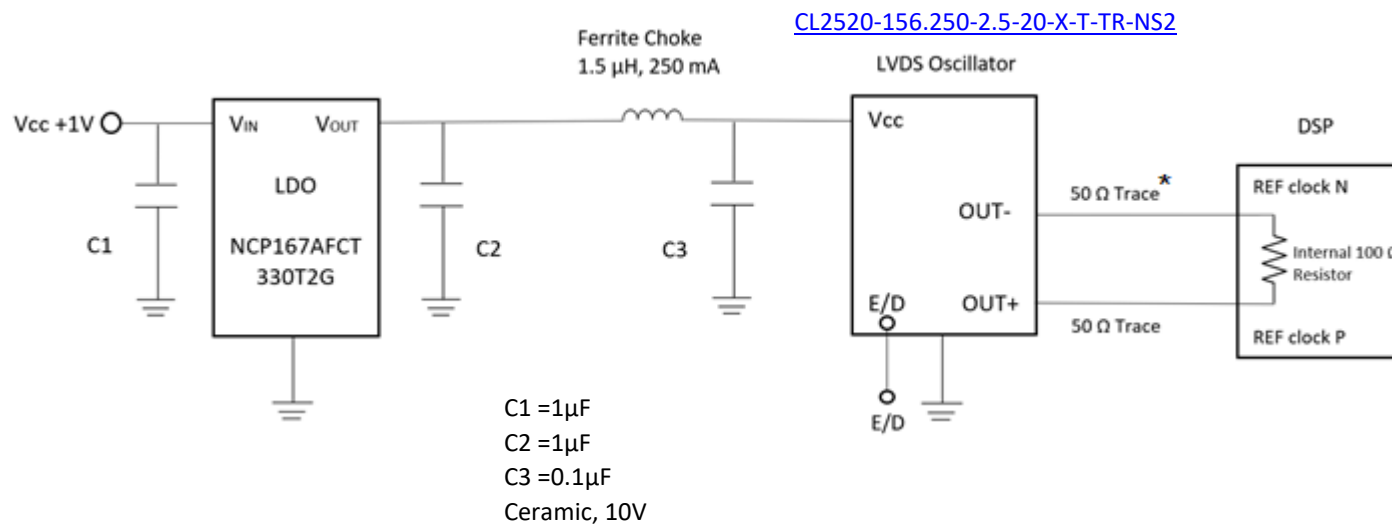

Example of [Raltron LVDS clock oscillators](#): CL2520-156.250-2.5-20-X-T-TR-NS2

***Note:** For LVDS signals, 50 Ω traces are needed in the circuit or test fixture. If the Ground Plane is on the same layer as the trace and there is also a Ground plane below on another layer, Coplanar Waveguide is recommended. If no Ground plane on the trace layer, then Microstrip is recommended. Many CAD programs for PCBA can be used to design a good 50 Ω trace. If the PCB design software does not have this capability, AppCAD is a free software available from Avago. Please see the following link:

<http://www.hp.woodshot.com/>

The AppCAD software has multiple options to design a 50 Ω trace in the “Transmission Lines” section.


Complete Circuit Configuration using LDO, choke and capacitors.

Offers excellent Power Supply Noise Reduction but uses excessive space and is costly because of the large number of components used. Recommended only for applications where space is not at a premium.

Circuit Configuration and PCB Layout Recommendations

Circuit Configuration 1 By-Pass Capacitors Only

[CL2520-156.250-2.5-20-X-T-TR-NS2](#)

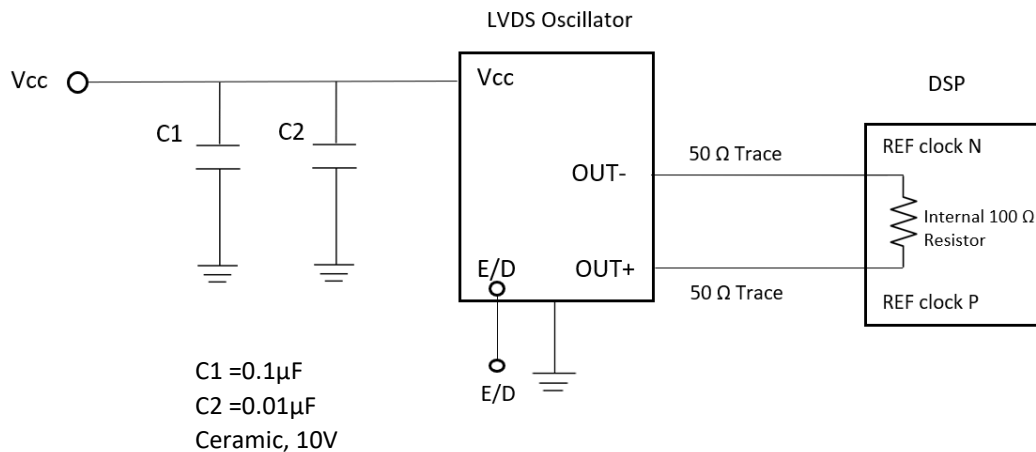


Simple Circuit Configuration using only filtering capacitors.

Offers reasonable Power Supply Noise Reduction based mostly on the Oscillator internal filtering but uses optimum space and is not costly because of the limited number of components used. Recommended only for applications where the on-board power supply is reasonably clean.

Circuit Configuration and PCB Layout Recommendations

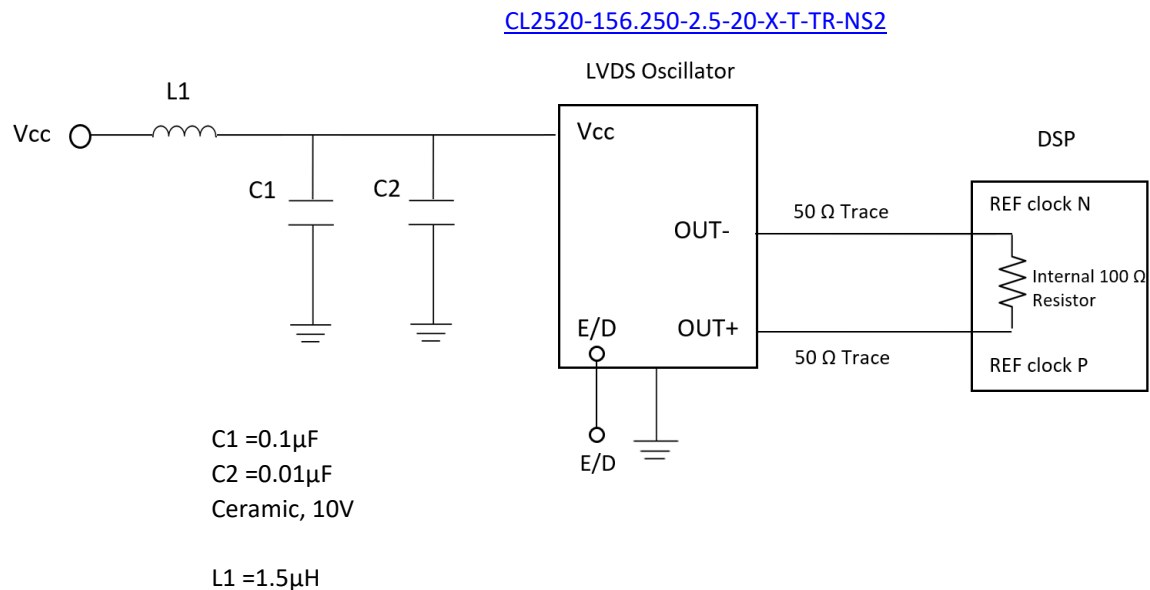Circuit Configuration 2 Ferrite Choke and By-Pass Capacitors




Simple Circuit Configuration using filtering capacitors and choke.

Offers better Power Supply Noise Reduction than Circuit Configuration 1 because of the additional noise suppression by the choke. Uses increased space and is more costly because of the additional component used. Recommended only for applications where the on-board power supply has an average noise level and space is not at a premium.

Circuit Configuration and PCB Layout Recommendations

Circuit Configuration 3 LDO and By-Pass Capacitors

[CL2520-156.250-2.5-20-X-T-TR-NS2](#)

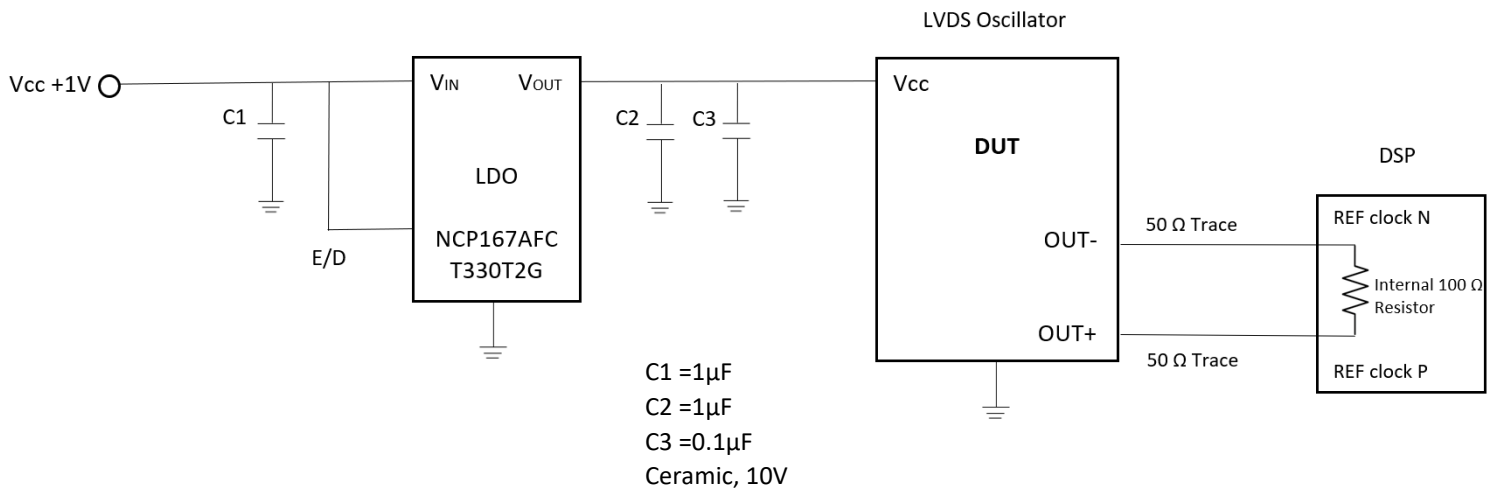



Simplified Circuit Configuration using LDO and filtering capacitors.

Offers better Power Supply Noise Reduction than Circuit Configuration 1 and 2 because of the superior noise reduction provided by the LDO. PCB space utilization is optimized because of the very small size of the LDO selected. This solution is recommended for applications such as small format optical transceivers where space is at a premium and increased PSRR is desired.

Phase Noise Test Circuit

C1=C4= 10 μ F
 C2=C5= 1 μ F
 C3=C6= 0.01 μ F
 Ceramic, 10V

[CL2520-156.250-2.5-20-X-T-TR-NS2](#)

 
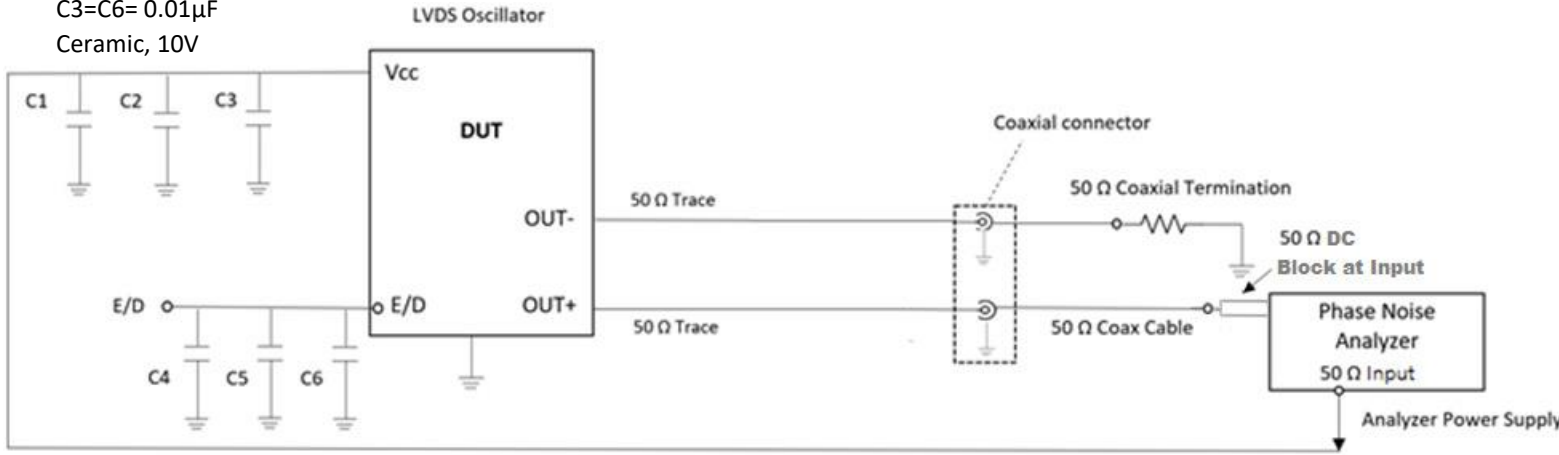


Correct oscillator phase noise plot obtained using above test circuit

Output Signal Integrity Test Circuit

- Use clean (low ripple) linear power supply
- Use two 50 Ω coax cables connected with the two clock oscillator outputs.
- Test: Output amplitude, rise & fall time, waveform symmetry

[CL2520-156.250-2.5-20-X-T-TR-NS2](#)

 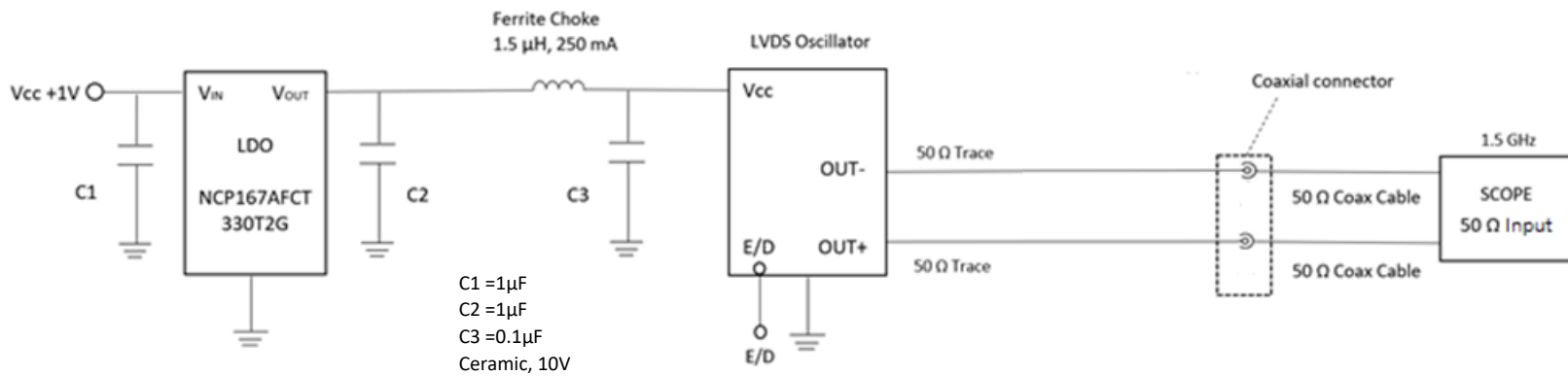

LVDS "OUT+" and "OUT-" Waveform in Eye Diagram
 (amplitudes of "OUT+" and "OUT-" around 360mV)

LVDS Oscillators Power Supply Noise Rejection Optimization

- Power supply noise rejection defines how well a circuit eliminates the effect of noise of various frequencies injected in it through its power supply input (Vcc pin). PSRR (Power Supply Rejection Ratio) is the ratio of the circuit input voltage variation to the circuit output voltage variation.
- Power supply noise rejection can be optimized by utilizing filtering circuitry. The most common filters are capacitors of various values, inductors(chokes) and linear regulators (LDOs- low drop-out regulators).
- For best results combinations of several or all these types of filters need to be used. The challenge is to find the best compromise solution between conflicting parameters: optimum PSRR which in general is proportional with the number of filtering components used, PCB space which is increasingly at premium and cost.
- The following Circuit Configurations 1-3 have been tested for PSRR performance using Raltron LVDS 156.250MHz 2520 oscillator PN [CL2520-156.250-2.5-20-X-T-TR-NS2](#)

Datasheet: [CL2520-156.250-2.5-20-X-T-TR-NS2](#)

The test consisted of injecting into the Oscillator Power Supply pin an AC waveform of 100 mV amplitude and measuring the Phase Noise Spurs produced at the Oscillator output for input signal frequencies of 10 kHz, 100 kHz, 1 MHz, and 10 MHz. The spurs amplitudes were then compared for the three proposed circuit configurations.


Raltron LVDS Oscillators Power Supply Noise Rejection Circuit Configurations

Circuit Configuration 1 By-Pass Capacitors Only

Test equipment: Phase Noise Analyzer Agilent E5052B, Signal Generator Agilent 33250A.
Condition: $V_{cc}=2.5V$

An AC sinewave signal is injected into the circuit at the point C indicated below and the waveform amplitude is measured to be 100mV at point C. The signal frequency is sequentially modified from 10kHz to 100kHz, 1MHz and 10MHz respectively and phase noise is measured in each case. The measurements are made at room temp, utilizing the circuit below,

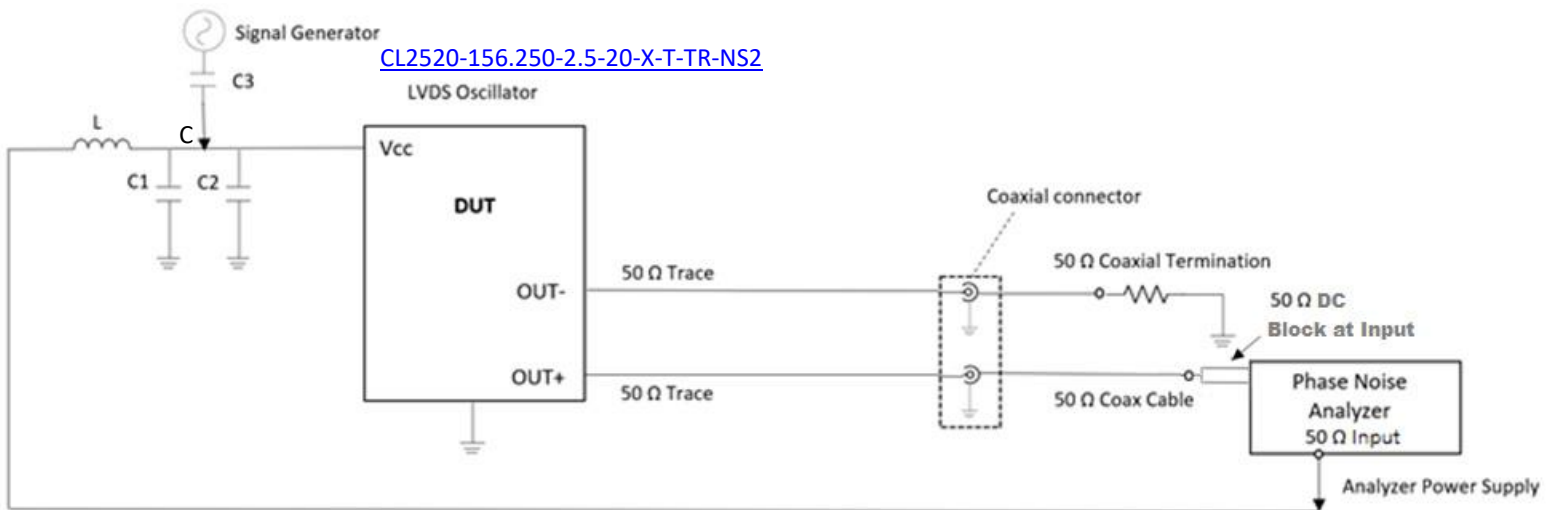The following components values are recommended: $C1=0.1\mu F$, $C2=0.01\mu F$, $C3=20.1\mu F$. The by-pass capacitors must be placed as close to V_{cc} & GND pins as possible. They are acting as low pass filters. The inductor L ($L=4.7\mu H$) is only part of the test fixture to prevent grounding of injected AC sinewave signal.



Offset Frequency from F_0	$F_n = 10kHz$	$F_n = 100kHz$	$F_n = 1 MHz$	$F_n = 10 MHz$
Phase Noise Spur Value Induced by Signal Generator [dBc/Hz]	-94.6	-120.56	-103.77	-148.18


Raltron LVDS Oscillators Power Supply Noise Rejection Circuit Configurations

Circuit Configuration 2 Ferrite Choke and By-Pass Capacitors

Test equipment: Phase Noise Analyzer Agilent E5052B, Signal Generator Agilent 33250A.
Condition: $V_{cc}=2.5V$

An AC sinewave signal is injected into the circuit at the point C indicated below and the waveform amplitude is measured to be 100mV at point C. The signal frequency is sequentially modified from 10kHz to 100kHz, 1MHz and 10MHz respectively and phase noise is measured in each case. The measurements are made at room temp, utilizing the circuit below,

The following components values are recommended: $C1=0.1\mu F$, $C2=0.01\mu F$, $C3=20.1\mu F$, $L1=1.5\mu H$. The by-pass capacitors must be placed as close to V_{cc} & GND pins as possible. The inductor $L1$ is improving the circuit PSRR by acting as a low pass filter in connection with the other capacitors. The inductor L ($L=4.7\mu H$) is only part of the test fixture to prevent grounding of injected AC sinewave signal.

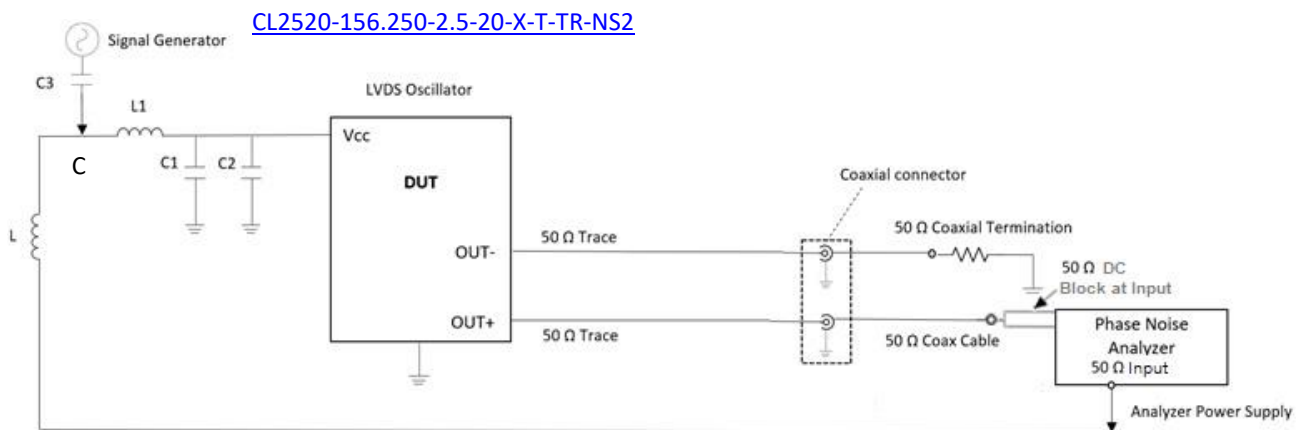

Offset Frequency from F_0	$F_n = 10kHz$	$F_n = 100kHz$	$F_n = 1 MHz$	$F_n = 10 MHz$
Phase Noise Spur Value Induced by Signal Generator [dBc/Hz]	-95.3	-122.56	-117.12	-156.30


Raltron LVDS Oscillators Power Supply Noise Rejection Circuit Configurations

Circuit Configuration 3 LDO and By-Pass Capacitors

Test equipment: Phase Noise Analyzer Agilent E5052B, Signal Generator Agilent 33250A.
Condition: $V_{CC}=2.5V$, LDO $V_{IN} = V_{CC}+1V$

An AC sinewave signal is injected into the circuit at the point C indicated below and the waveform amplitude is measured to be 100mV at point C. The signal frequency is sequentially modified from 10kHz to 100kHz, 1MHz and 10MHz respectively and phase noise is measured in each case. The measurements are made at room temp, utilizing the circuit below,

The following components values are recommended: $C1=1\mu F$, $C2=0.1\mu F$, $C3=20.1\mu F$, $C4=1\mu F$. The by-pass capacitors must be placed as close to V_{CC} & GND pins as possible. The inductor L ($L=4.7\mu H$) is only part of the test fixture to prevent grounding of injected AC sinewave signal. The use of an LDO (Low Dropout Regulator) between the on-board power supply output and the oscillator V_{CC} pin is recommended. The ON Semiconductor LDO P.N. CNP167AFCT330T2G has been successfully tested for this purpose. The LDO performance is superior to the performance of filters used in the previous solutions.

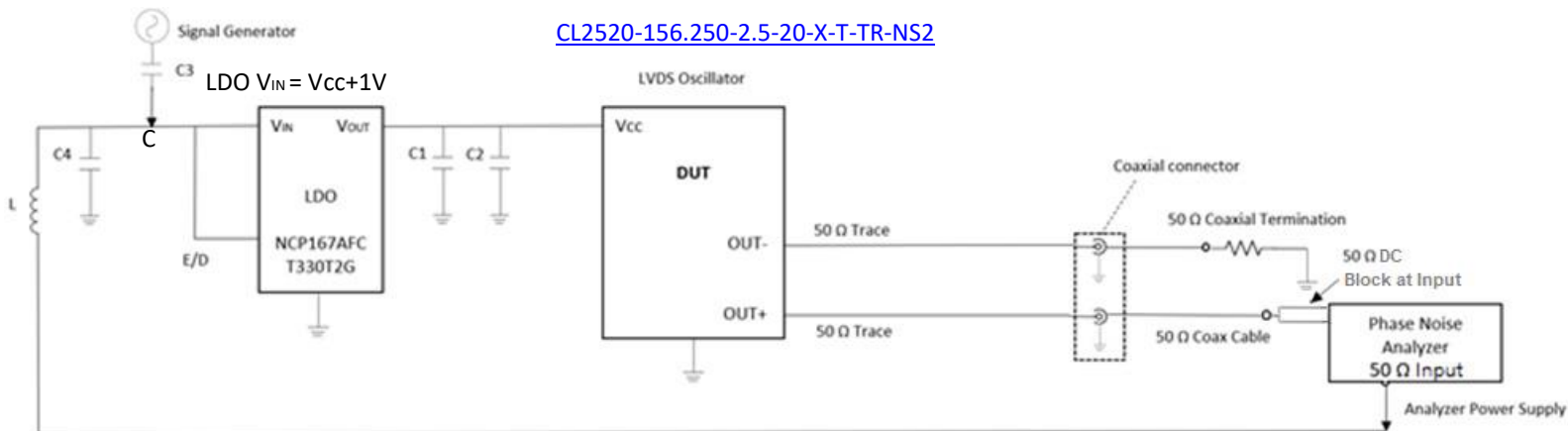

Offset Frequency from F_0	$F_n = 10kHz$	$F_n = 100kHz$	$F_n = 1 MHz$	$F_n = 10 MHz$
Phase Noise Spur Value Induced by Signal Generator [dBc/Hz]	-145.20	-153.50	-158.10	-160.00

Raltron LVDS Oscillators Power Supply Noise Rejection Circuit Configurations

Comparison Between the Three Proposed Circuit Configurations

Solutions	Recommended Components	Parameter	CL2520-156.250-2.5-20-X-T-TR-NS2			
			Fn =10kHz	Fn =100kHz	Fn =1 MHz	Fn =10 MHz
		Frequency Offset from Fo				
#1 By-pass capacitors	0201 Caps: 0.6x0.3x0.3mm		-94.60	-120.56	-103.77	-148.18
#2 Ferrite Choke and by-pass capacitors	Ferrite Choke: 1.7x0.9x0.9mm 0201 Caps: 0.6x0.3x0.3mm	Phase Noise Spur Amplitude [dBc/Hz] Induced by Input Sinewave Signal of 100 mV	-95.30	-122.56	-117.12	-156.30
#3 LDO and by-pass capacitors	LDO PN. ON SEMI NCP167AFCT330T2G: 0.65x0.65x0.33mm 0201 Caps: 0.6x0.3x0.3mm		-145.20	-153.50	-158.10	-160.00

Recommendations

Raltron LVDS oscillators show an excellent intrinsic PSRR and could be used with only external filtering capacitors in most cases where the available power supply is reasonable clean.

However, for increased performance in case of sub-average power supply output noise level, the use of an LDO is recommended.

ON SEMI LDO PN NCP167AFCT330T2G is offering a low- cost solution for an excellent PSRR and a very small size package compatible with the smallest sized applications (example QSFP-DD optical transceivers)

Datasheet: [NCP167AFCT330T2G](#)

Circuit Configuration 3 is recommended for optimum PSRR/size/cost performance when the available power supply noise level is not optimum.